

Experiment → 10

Date → 8th October 2020

Aim → Applications of flip-flop

i) Three-bit binary counter using J.K flip-flop

ii) Frequency Divider

Apparatus required →

Source	Specification	Quantity
1) CD 4000	CD 4027A [JK]	7
2) source	digiclock	2
3) 7400	7400 [and gate]	1
4) Power/Ground	• \$D-HI • \$D-LO	2 4

Present state			Next state			Flip-flop inputs						
clk	Q_C	Q_B	Q_A	Q_{C+1}	Q_{B+1}	Q_{A+1}	J_C	K_C	J_B	K_B	J_A	K_A
0	0	0	0	0	0	1	0	X	0	X	1	X
1	0	0	1	0	1	0	0	X	1	X	X	1
2	0	1	0	0	1	1	0	X	X	0	1	X
3	0	1	1	1	0	0	1	X	X	1	X	1
4	1	0	0	1	0	1	X	0	0	X	1	X
5	1	0	1	1	1	0	X	0	1	X	X	1
6	1	1	0	1	1	1	X	0	X	0	1	X
7	1	1	1	0	0	0	X	1	X	1	X	1

$Q_C \backslash Q_B Q_A$	00	01	11	10
0	0	0	1	0
1	X	X	X	X

$$J_C = Q_B Q_A$$

$Q_C \backslash Q_B Q_A$	00	01	11	10
0	X	X	X	X
1	0	0	1	0

$$K_C = Q_B Q_A$$

$Q_C \backslash Q_B Q_A$	00	01	11	10
0	0	1	X	X
1	0	1	X	X

$$J_B = Q_A$$

$Q_C \backslash Q_B Q_A$	00	01	11	10
0	X	X	1	0
1	X	X	1	0

$$K_B = Q_A$$

$Q_C \backslash Q_B Q_A$	00	01	11	10
0	1	X	X	1
1	1	X	X	1


$$J_A = 1$$

$Q_C \backslash Q_B Q_A$	00	01	11	10
0	X	1	1	X
1	X	1	1	X


$$K_A = 1$$

Q_n	Q_{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

} Excitation Table of JK flip-flop

 


 3-bit ripple-carry adder using 74181 ALU chips.



Run-to time $\rightarrow 20 \text{ ms}$

Frequency divider

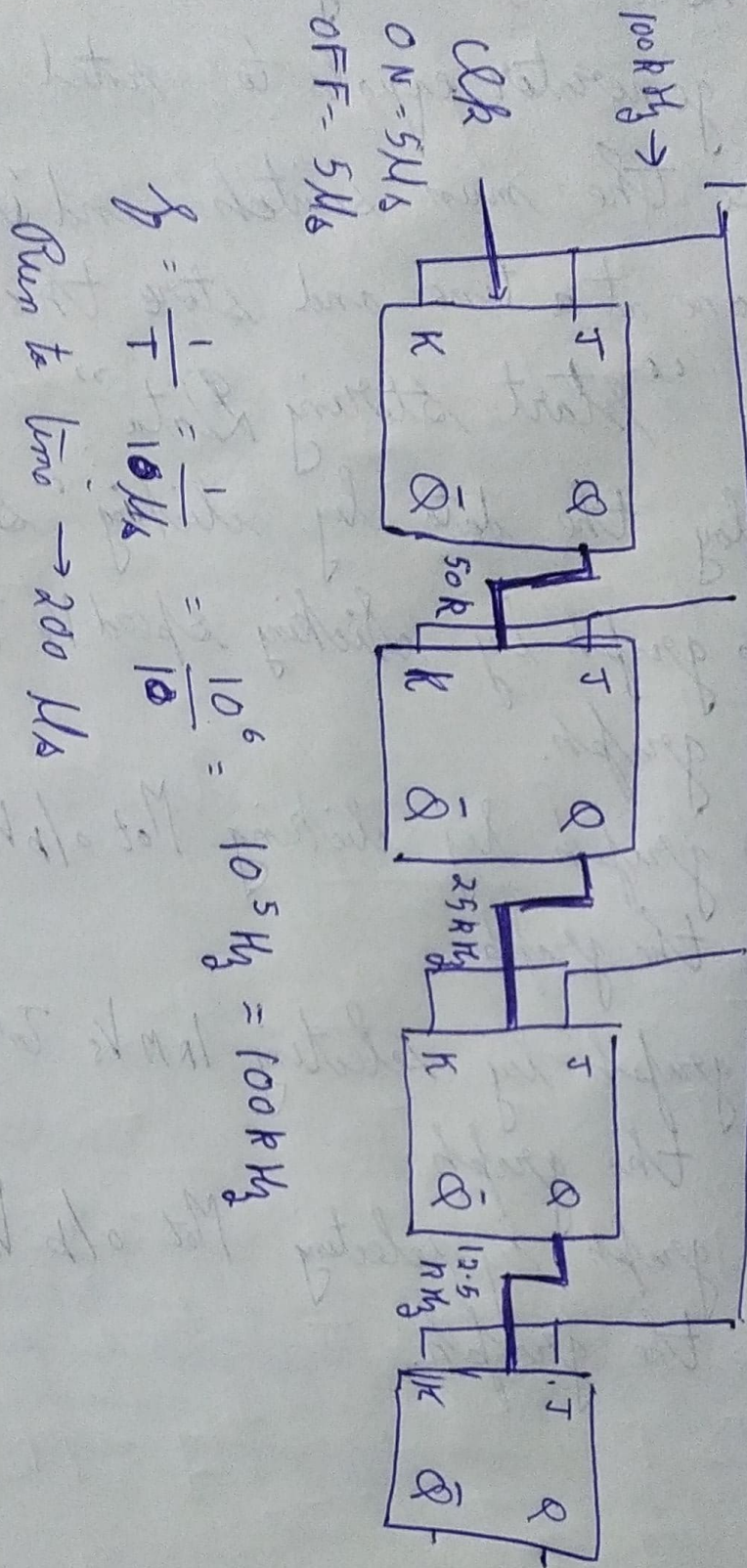

$$f = \frac{1}{T} = \frac{1}{10 \mu s} = \frac{10^6}{10} = 10^5 \text{ Hz} = 100 \text{ kHz}$$

Run to line $\rightarrow 200 \text{ MHz}$

Result \rightarrow We need to set settings as transient along with option of gate levels in, inside digi state as 0 instead of X in order for it to store the previous state values.