

Ex: No:3

Name:-Aadi Mahajan

Registration number:-19BEE0032

Aim: **Design of Half wave and full wave rectifier using op-amp**

Apparatus required:

Name	Specialization	Quantity
Resistor	1k	8
Op-amp	LM-741	2
Voltage source	V sin	2
Diode	D1N4001	4

Circuit diagram/ Calculation/equation:

a)Half-wave rectifier

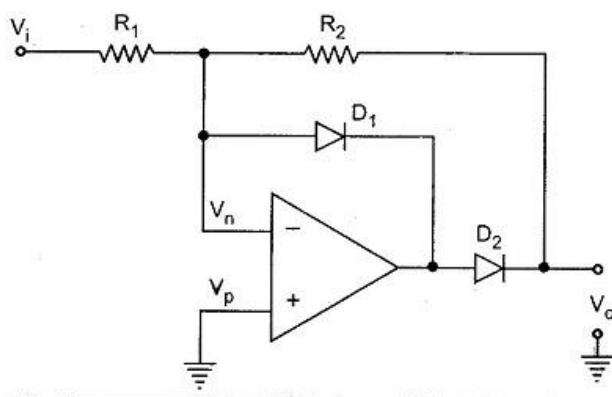


Fig. 2.60 Inverting half wave rectifier

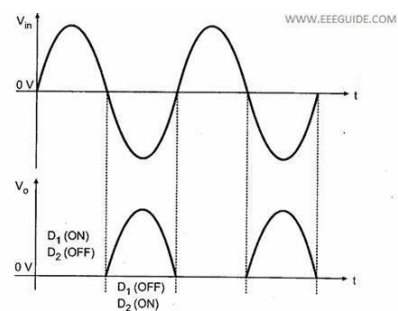



Fig. 2.61 Input and output waveforms for inverting half wave rectifier

$$R_1=R_2=R=1k\Omega$$

$$V_{amp}=1$$

$$f=50Hz$$


b) full wave rectifier

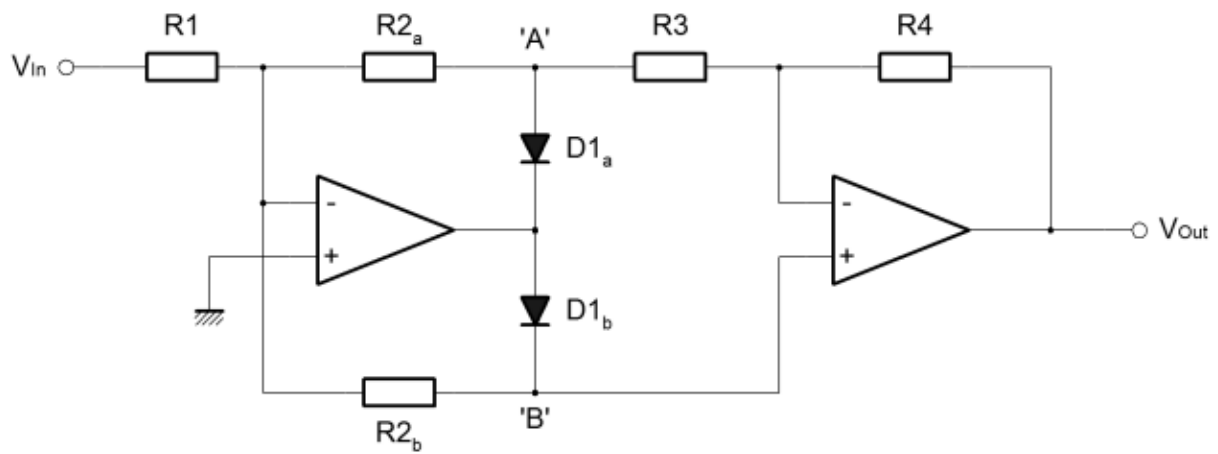



$$R1=R2_a=R2_b=R3=R4=R=1k\Omega$$

$$V_{amp}=1$$

$$f=50Hz$$

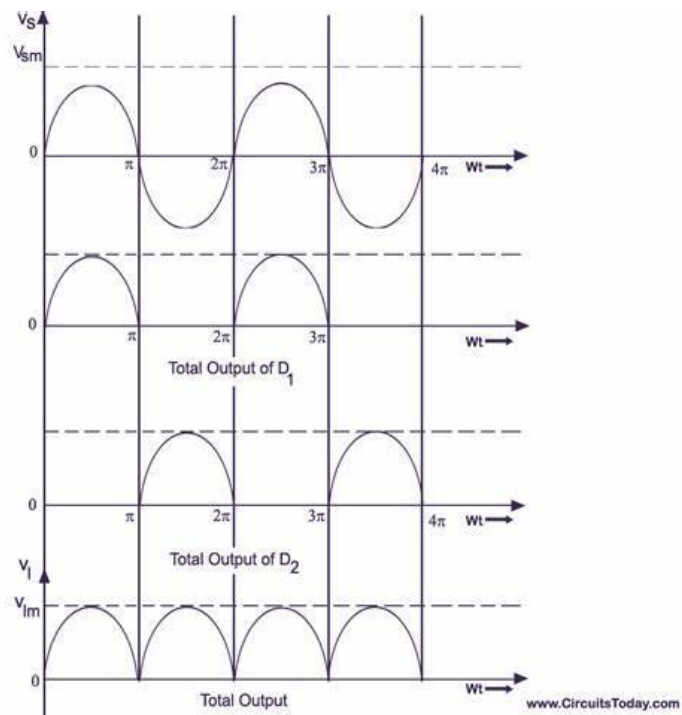


Simulation diagram:

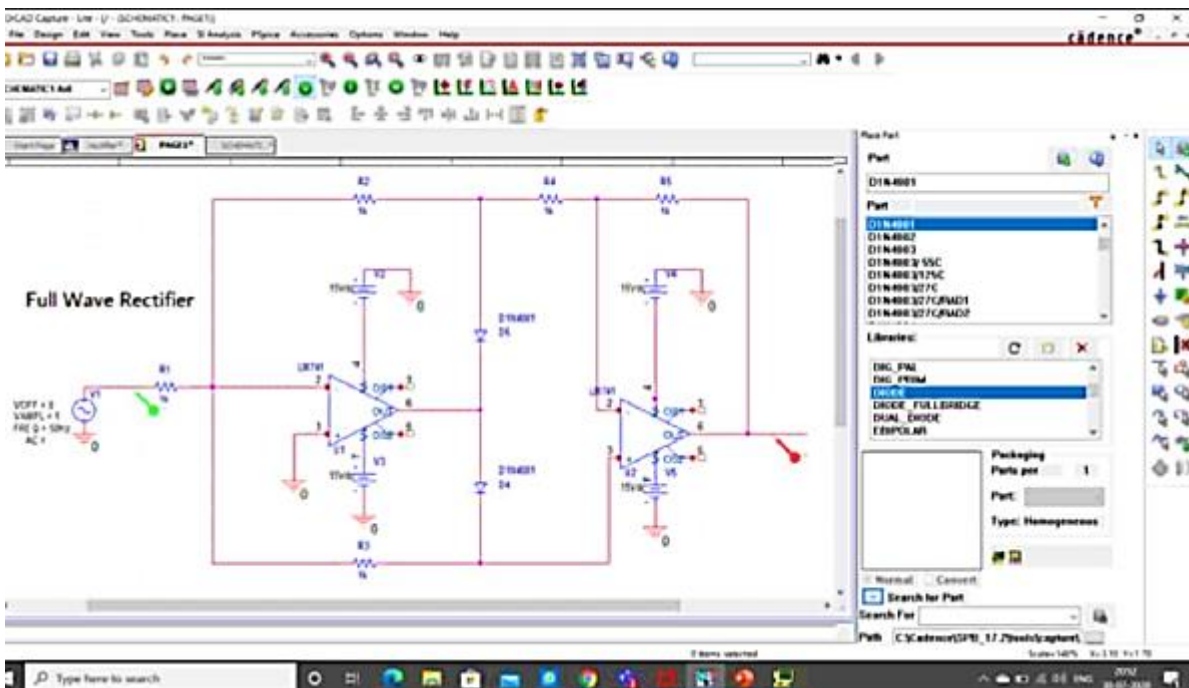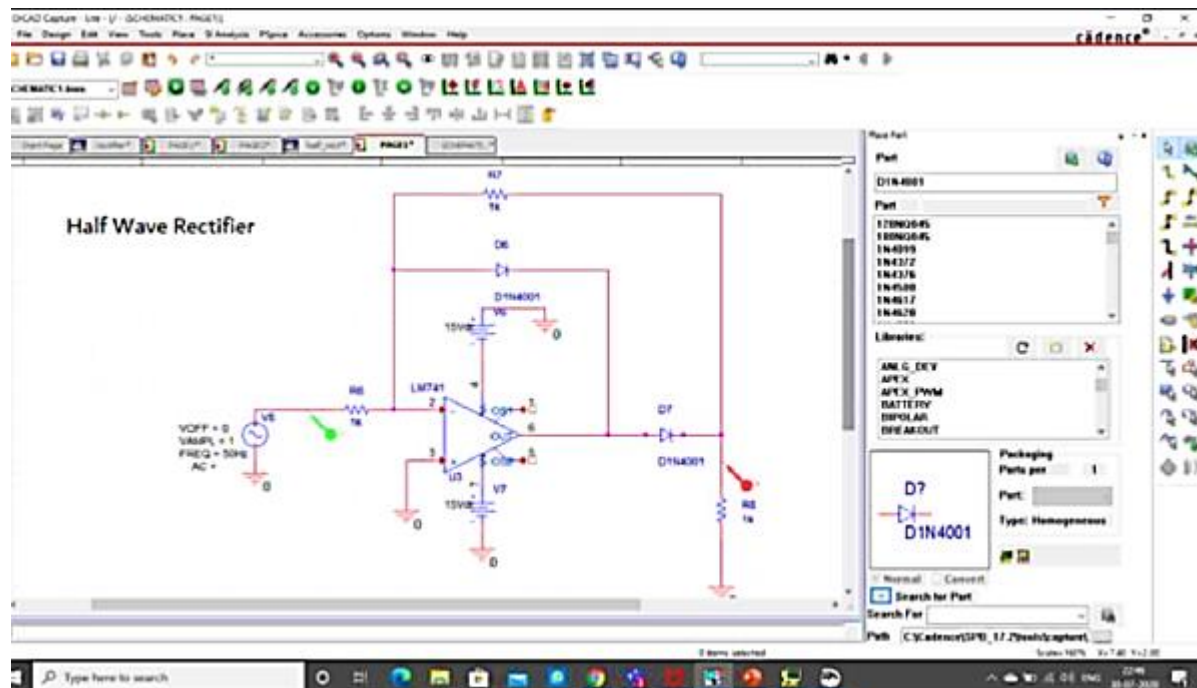

Output graph:

## FULL-WAVE RECTIFIER

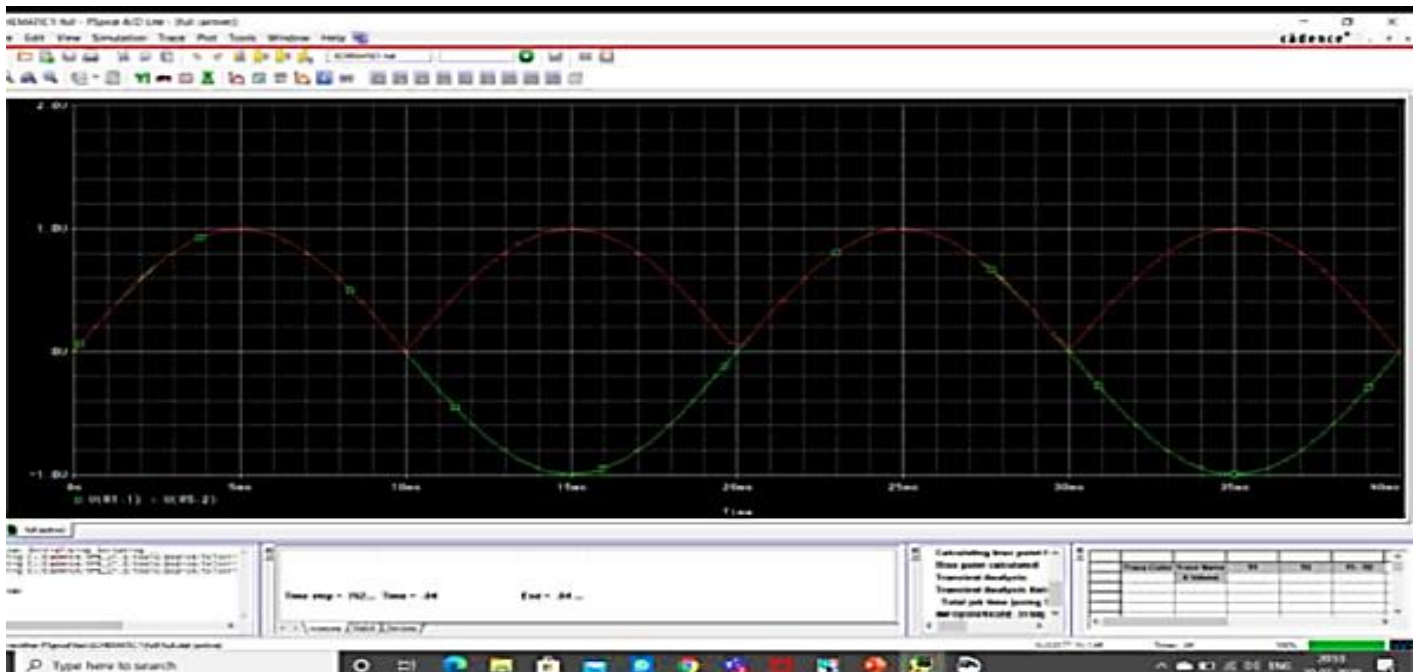

## HALF-WAVE RECTIFIER



**Result and inference:** half wave use one op-amp, while full wave use two op-amps. The problem with using only diode still persists as output is not constant like a dc one but this output can be used for other purposes.

