

Exp. no  $\rightarrow$  4

Hadi Mahajan  
19BEE0032


Date  $\rightarrow$  20 August 2020

Aim  $\rightarrow$  Design a square wave & triangular wave generator for a frequency of 1 kHz.




Apparatus required  $\rightarrow$

Name of Item	Specification	Quantity
Op-amp	LM-741	2
Resistor	10 k $\Omega$	2
	4.5 k $\Omega$	1
	1 k $\Omega$	2
Capacitor	0.1 $\mu$ F	2

Circuit diagram  $\rightarrow$

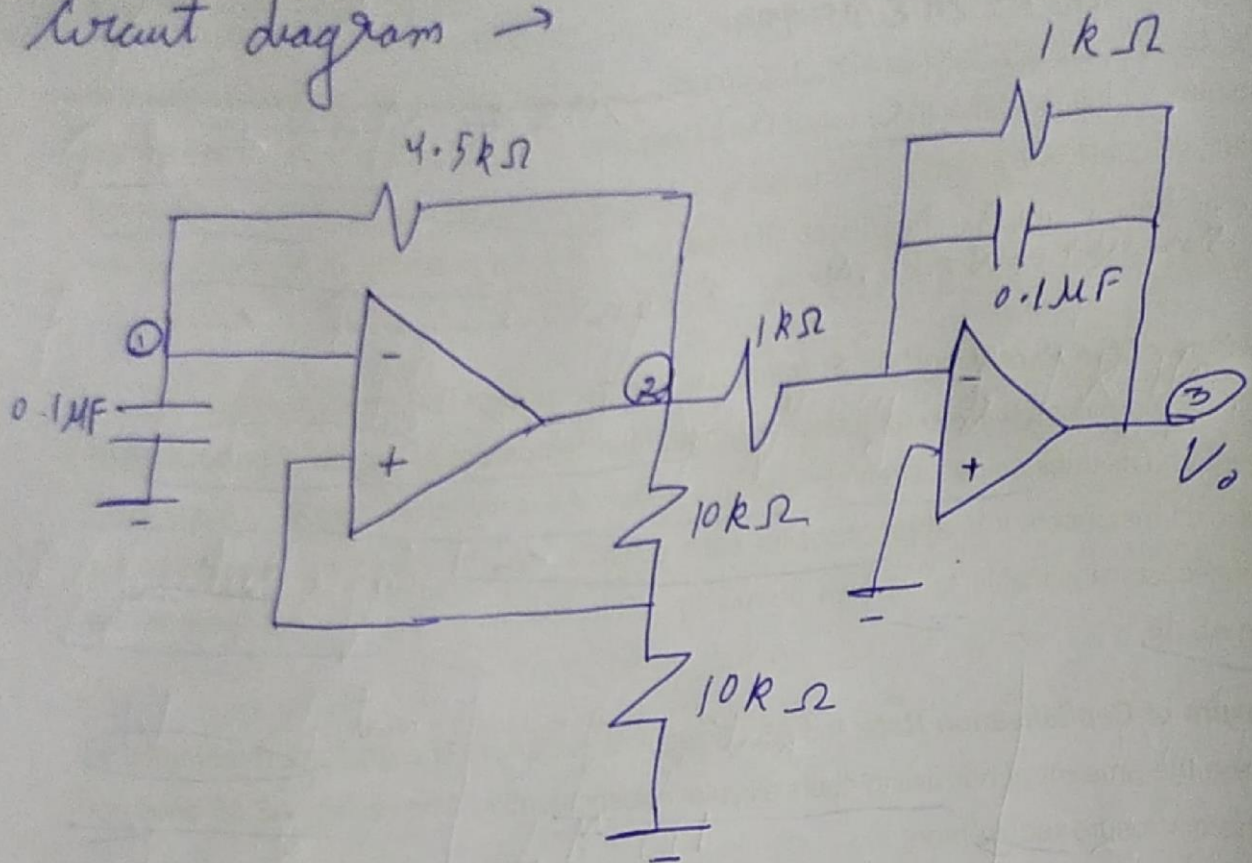

Model graph  $\rightarrow$

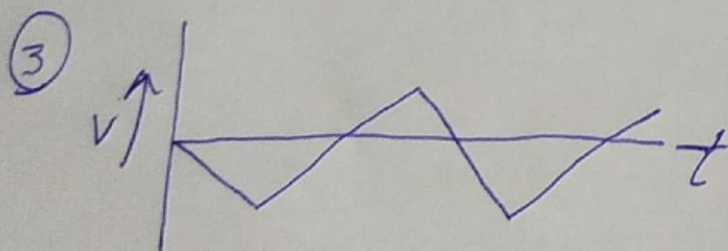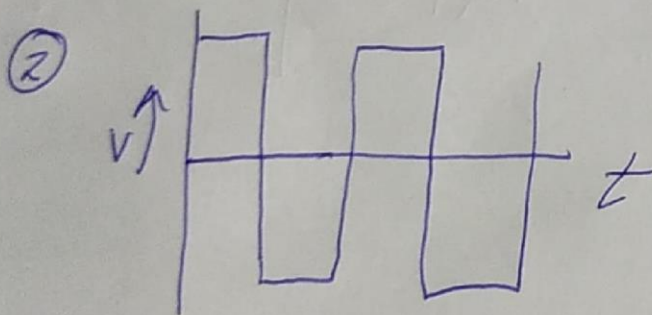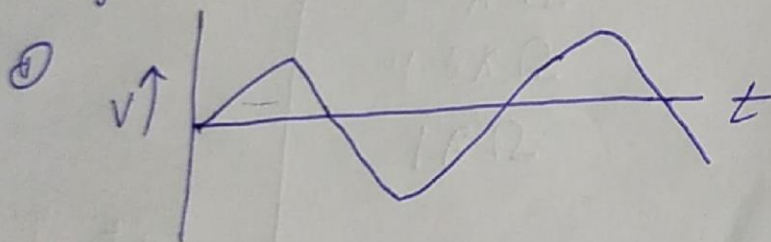



Calculations  $\rightarrow F = 1 \text{ kHz}$

$$\Rightarrow T = 1 \text{ ms} = \frac{1}{F}$$

$$\beta = \frac{R_2}{R_1 + R_2} = \frac{10 \text{ k}}{10 \text{ k} + 10 \text{ k}} = 0.5$$

$$T = 2RC \ln \left( \frac{1+\beta}{1-\beta} \right)$$

$$= 2RC \ln \left( \frac{1.5}{0.5} \right)$$



$$= 2.197 RC$$

Assuming  $C = 0.1 \text{ nF}$

$$1 \text{ ms} = 2.197(R) \times (0.1 \times 10^{-6})$$


$$\Rightarrow R = \frac{10^{-3}}{2.197 \times 0.1 \times 10^{-6}} = 4.5 \text{ k}\Omega$$

SIMULATION DIAGRAM:-

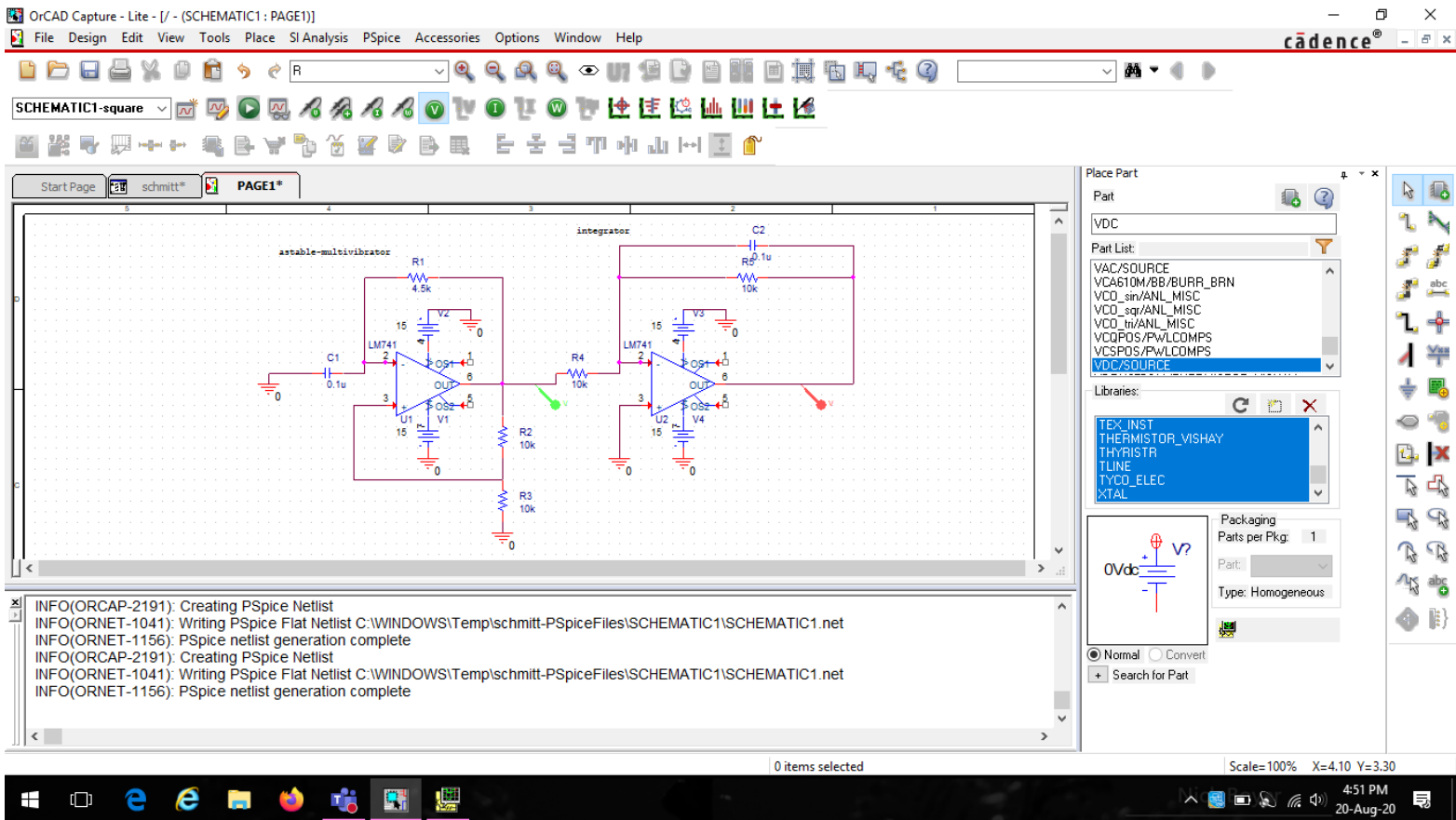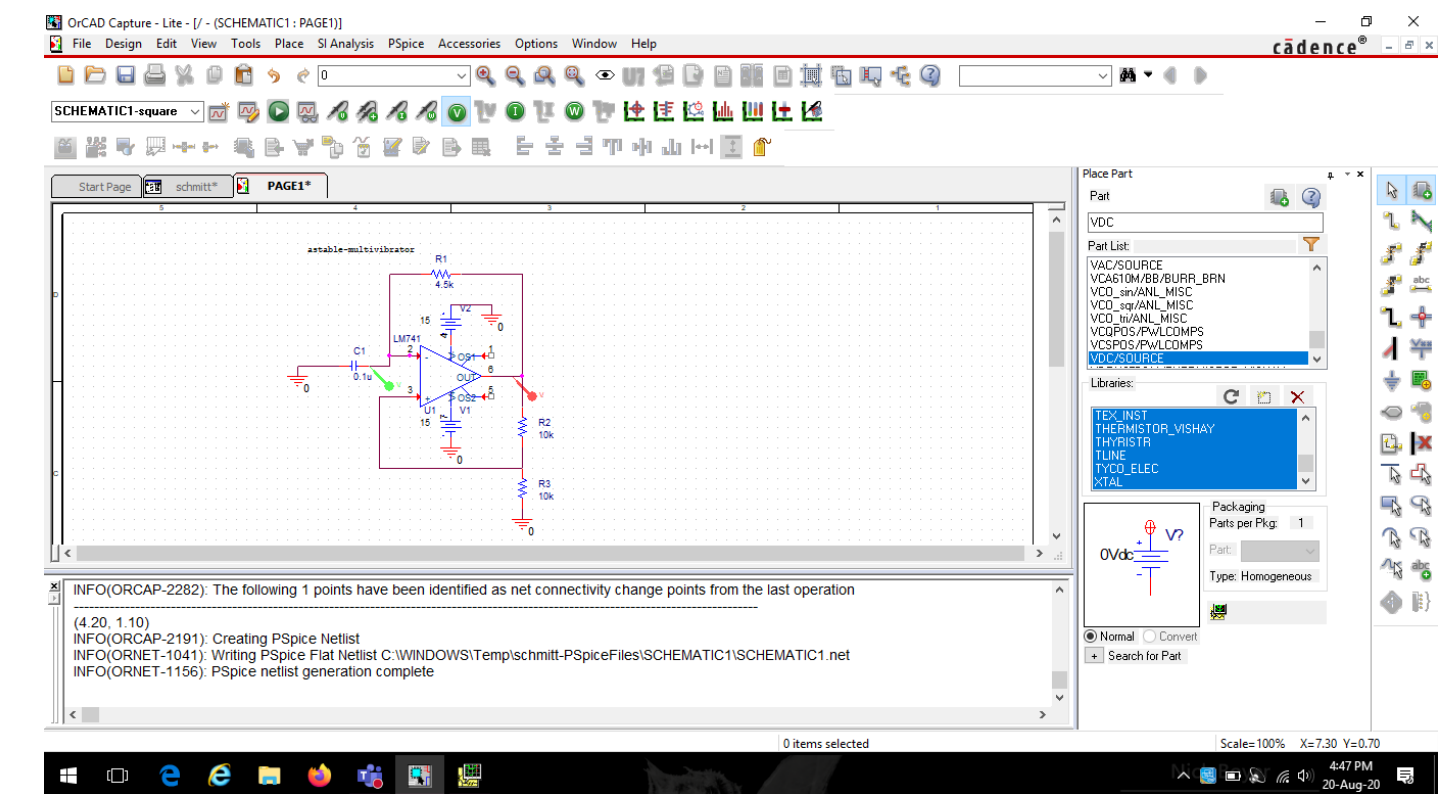


OUTPUT GRAPHS :-

(Graph after astable-multivibrator)

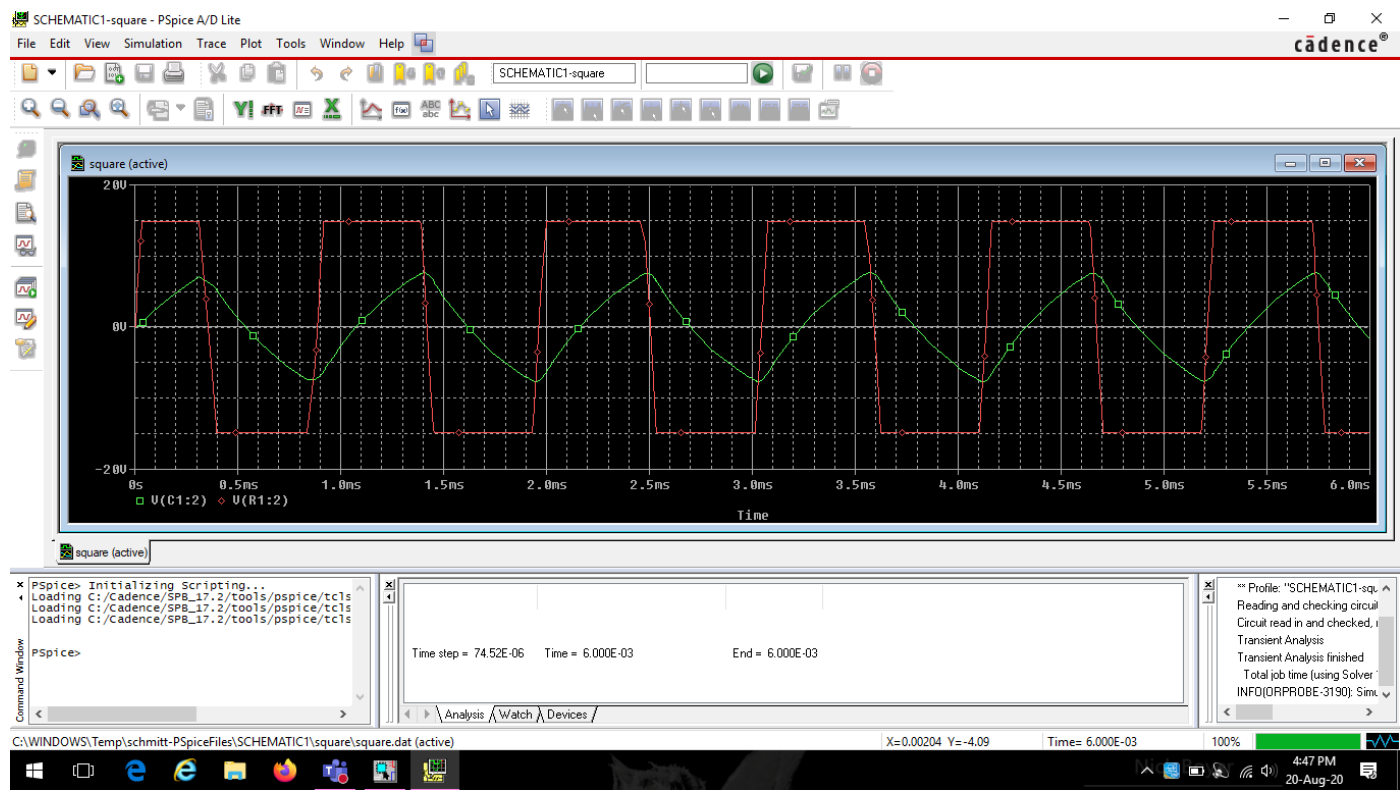

(Graph after integrator)

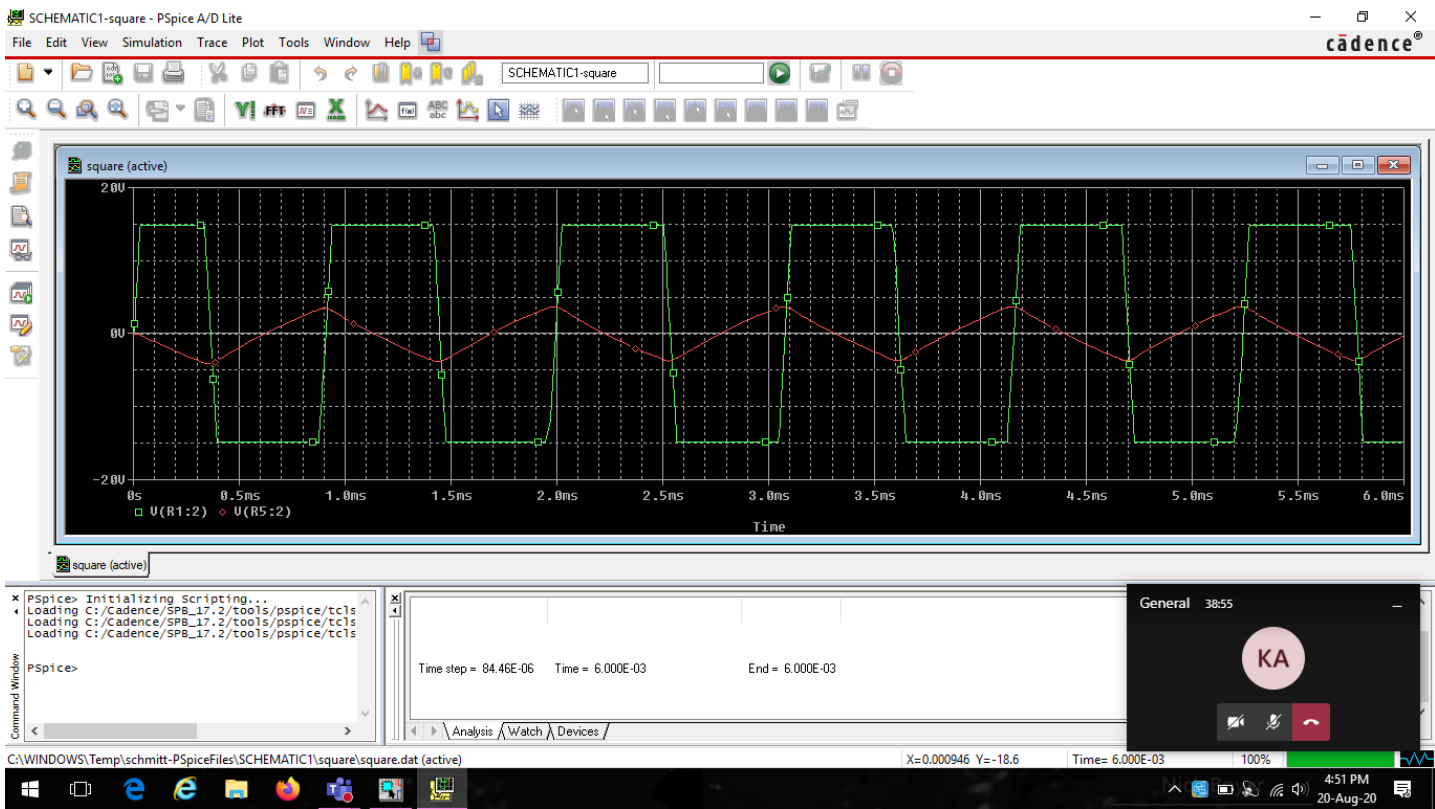



Result & Inference  $\rightarrow$  The input & output signals have a phase shift of  $180^\circ$  & the amplitude of output is also decreased.