

Exp no - 1

19BEE0032

Date → 24/07/2020


Pradi Mahajan

Aim → Design of inverting and non-inverting amplifier using Op-Amp IC 741.

Apparatus required →

Name of item	Specification	Quantity
Op-amp	IC 741 [LM741]	2
Resistor	$1\text{ k}\Omega$	4
Voltage sources	DC → 15V	4
	AC → amp → 1 $f \rightarrow 50$	2


Circuit diagram →

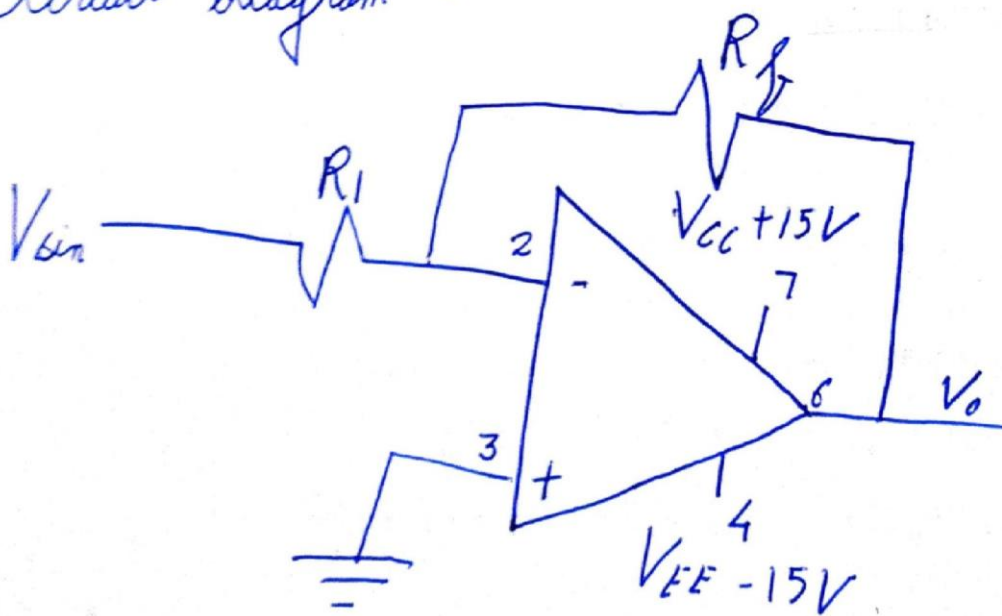


$$V_o = -\frac{R_f}{R_i} V_i$$

Phase shift between input and output = 180°

Model graph \rightarrow

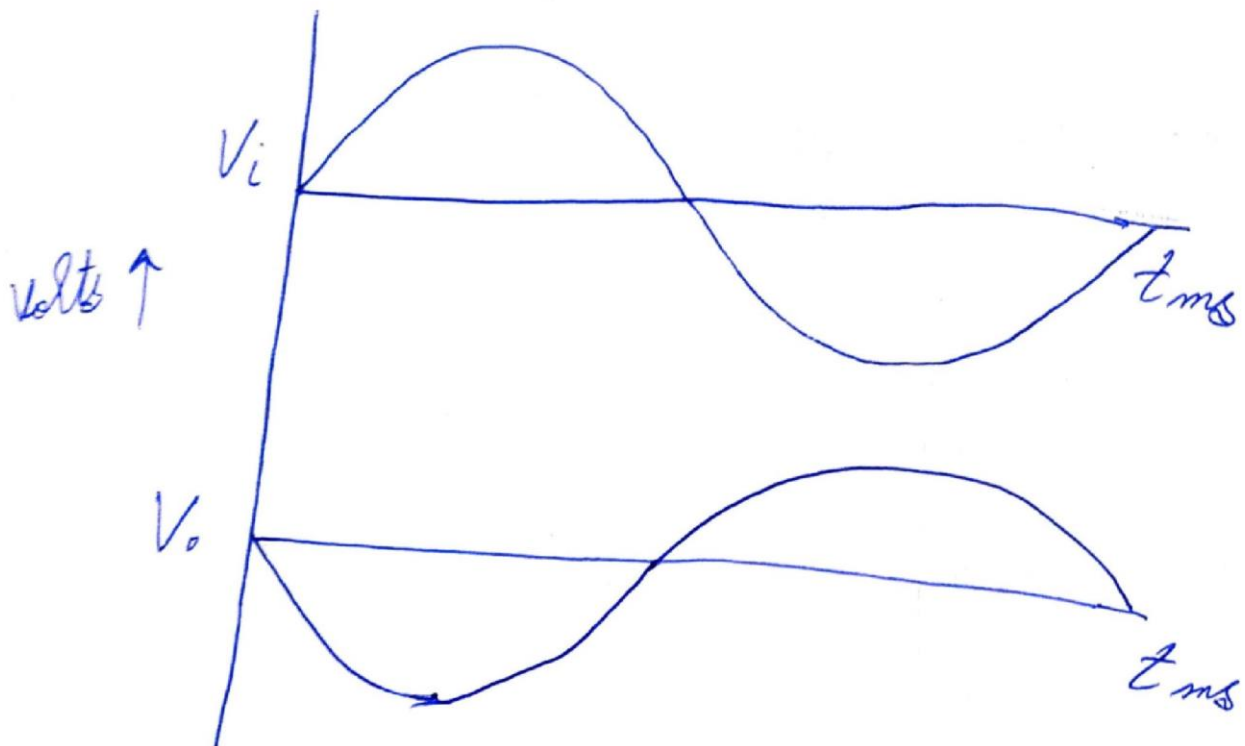


Non-inverting amplifier

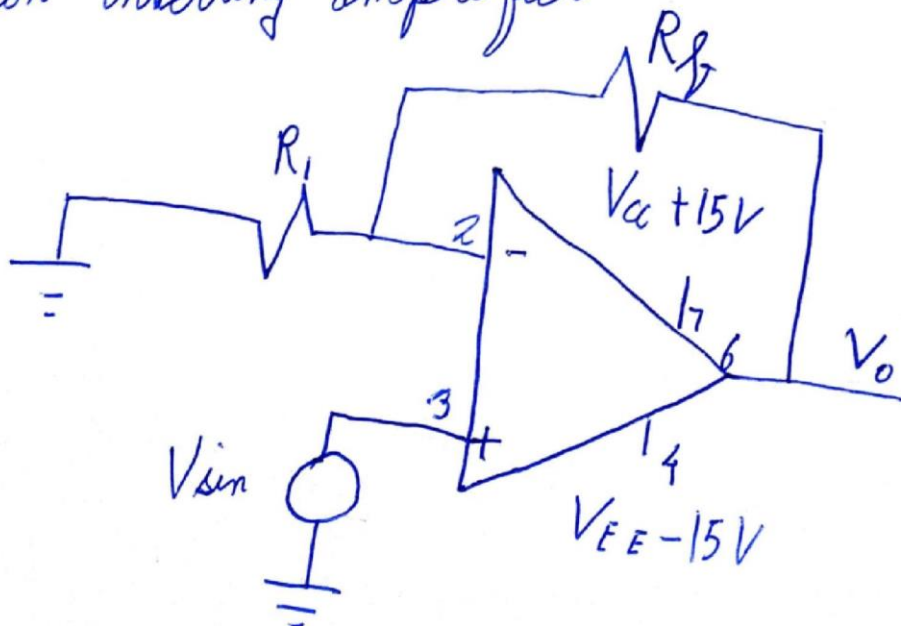


$$V_o = \left(1 + \frac{R_f}{R_i}\right) V_i$$

Phase difference between input and output = 0°


Model graph

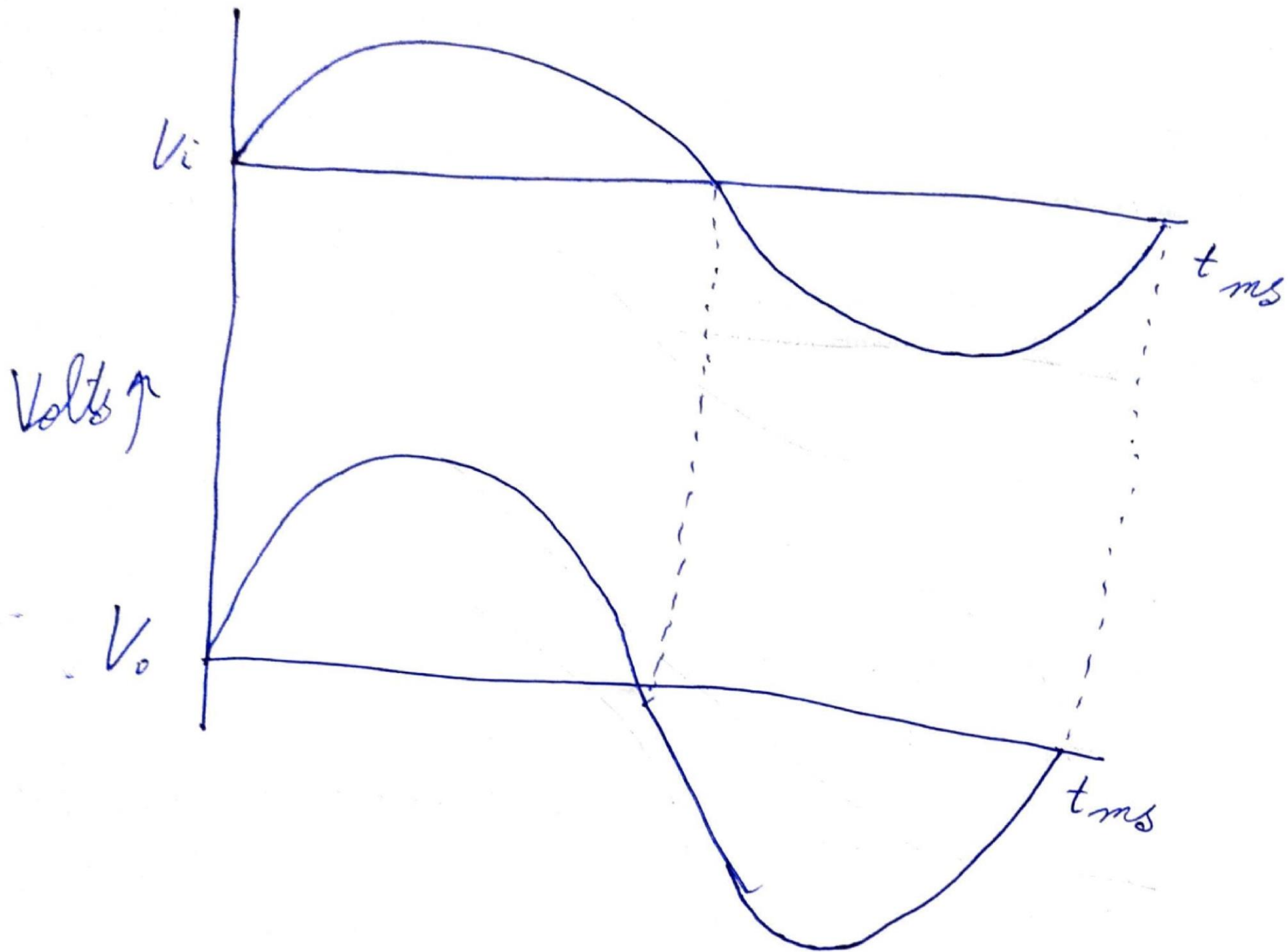


Simulation diagram:-

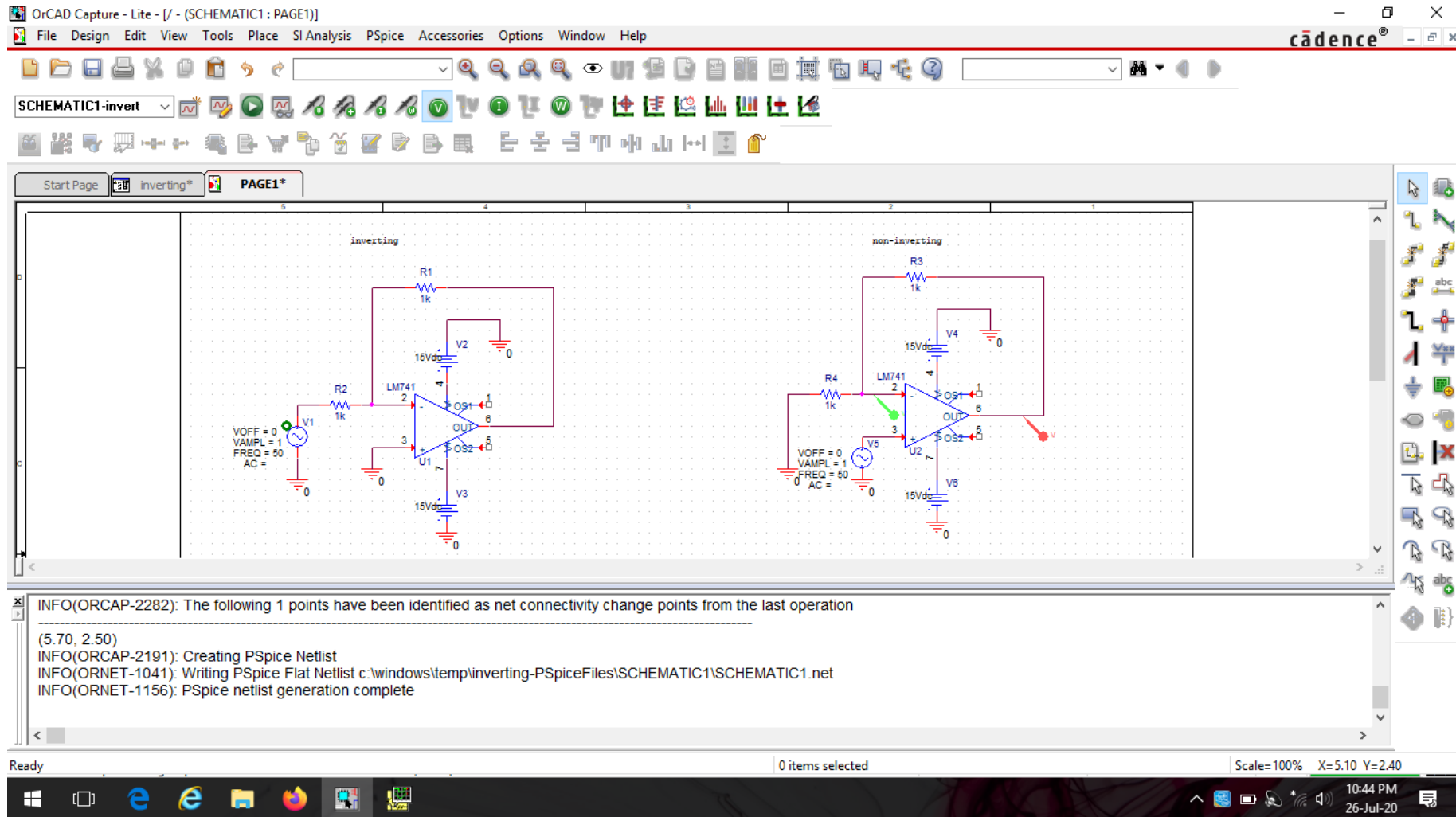

Graph:-

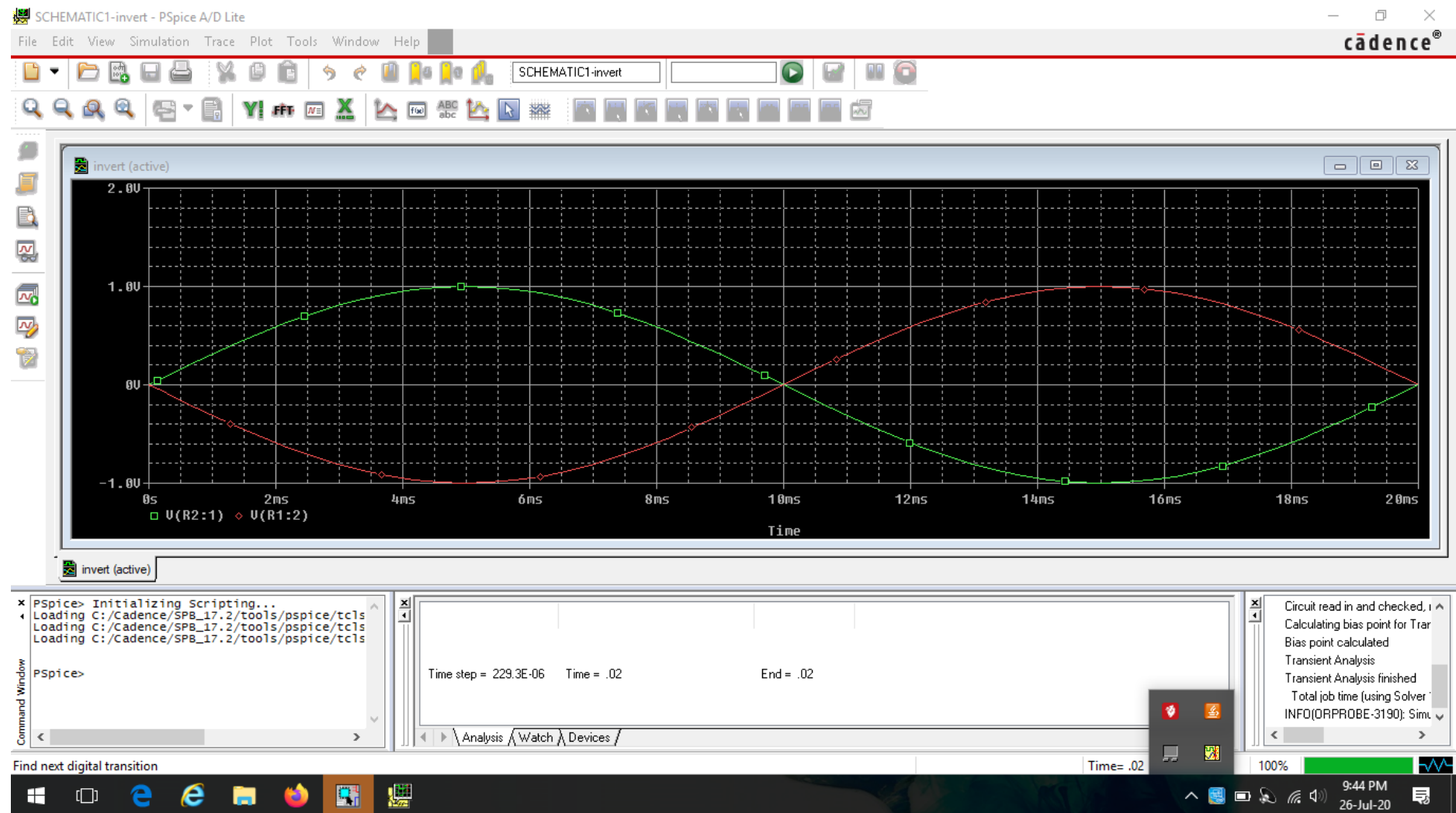

(INVERTING AMPLIFIER)

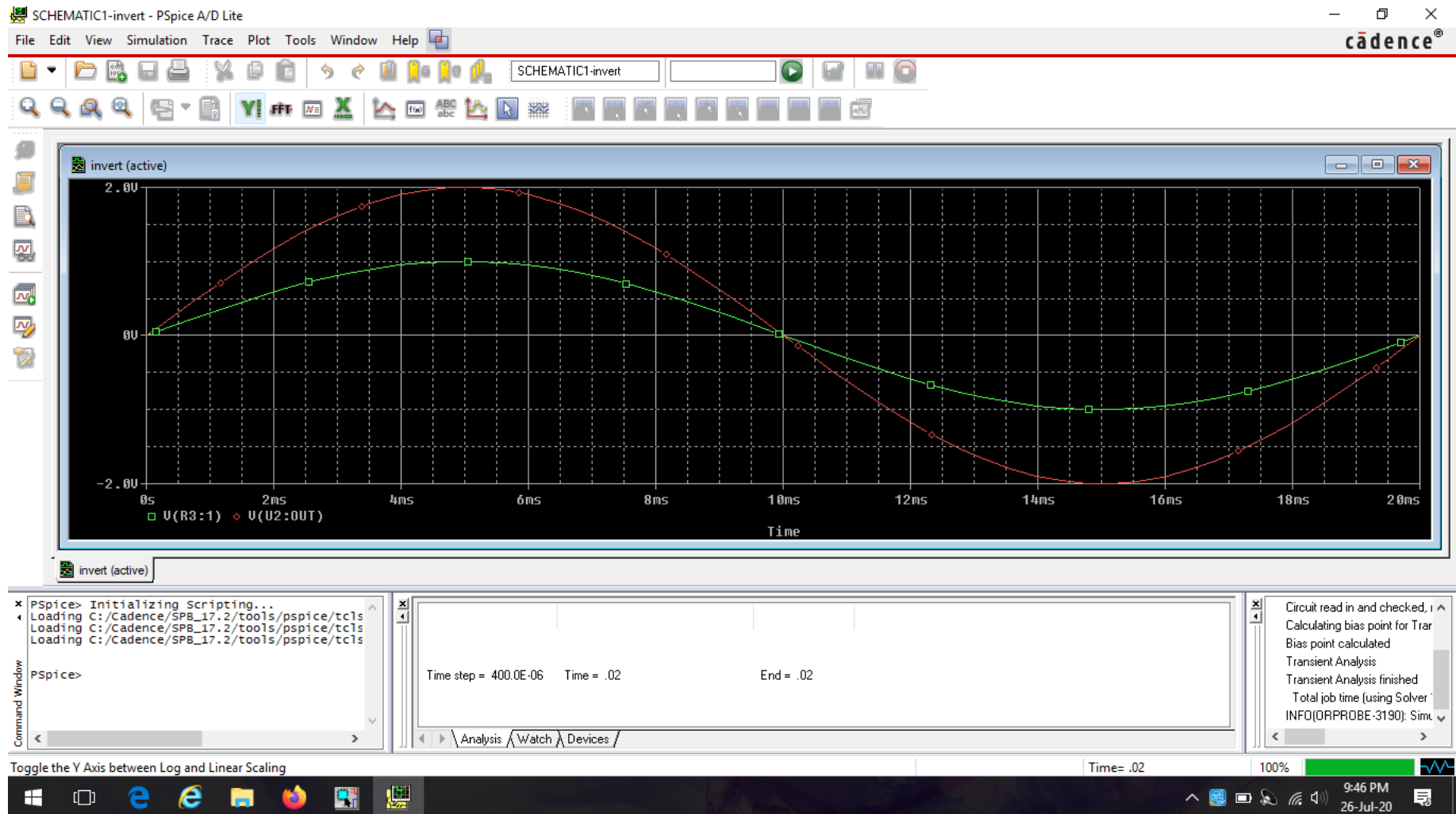

(NON INVERTING AMPLIFIER)

Result \rightarrow The output of inverting amplifier has a phase shift of 180° with no increase in amplitude while of non-inverting has a phase shift of 0° with an increase of amplitude of R_f/R_i .

Inference \rightarrow If $R_f = 0$ in non-inverting it becomes voltage follower, i.e., amplitude increase is 0.